

# 1 Why Pipelining?

The datapath design that we implemented for Project 1 was, in fact, grossly inefficient. By focusing on increasing throughput, a pipelined processor can get more instructions done per clock cycle. In the real world, that means higher performance, lower power draw, and most importantly, happy customers!

## 2 Project Requirements

In this extra credit project, you will make a pipelined processor that implements the LC-901 ISA. There will be five stages in your pipeline:

1. **IF** - Instruction Fetch
2. **ID/RR** - Instruction Decode/Register Read
3. **EX** - Execute (ALU operations)
4. **MEM** - Memory (both reads and writes with memory)
5. **WB** - Writeback (writing to registers)

Before you move on, read Appendix A: LC-901 Instruction Set Architecture to understand the ISA that you will be implementing. This is the same ISA that we had you implement for Project 1. The only difference here that you will need to worry about is the new I-MEM and D-MEM instead of just a single block of memory. Understanding the instructions supported by your ISA will make designing your pipeline much easier. We provide you with a CircuitSim file with the some of the structure laid out and some included components (subcircuits) that you are free to use as you see fit.

## 3 Building the Pipeline

First, you will have to build the hardware to support all of your instructions. You will have to make each stage such that it can accommodate the actions of all instructions passing through it. Use the book (Ch. 5) to get an idea of what the pipeline looks like and to understand the function of each stage before you start building your circuits.

### 1. IF Stage

The IF stage is responsible for:

- Getting the instruction from I-MEM at location PC
- Updating the PC

For normal sequential execution, we would update the PC by incrementing it by 1. Notice, however, that this may not be the case when executing a branch or JALR instruction. Hence, you will likely need to multiplex which value is used to update the PC. I-MEM has 16 address bits.

### 2. ID/RR Stage

The ID/RR stage is responsible for:

- Decoding the instruction
- Reading the appropriate registers

Please look at Appendix A: LC-901 Instruction Set Architecture in order to understand the instruction formats! You will be provided a dual ported register file (DPRF), which allows you to read from two registers and write one register all at the same time.

Some of the instructions require both inputs into the ALU to be values pulled from the DPRF. However, other instructions contain a value within the instruction, such as an `immval20`, `offset20`, or `PCoffset20` field. You may either pass all of these possible values to the next stage (requires bigger buffer registers), or condense them into just the values needed to execute the instruction in the following cycles (requires more logic, but buffer size can be optimized).

### 3. EX Stage

The EX stage is responsible for:

- Performing all necessary arithmetic and logic calculations
- Resolving any branch or JALR instructions

In the Execute (EX) stage, you will perform any arithmetic computations required by the instruction. This stage should host a complete ALU to perform the actual adding or NANDing as required by the instruction. For memory access instructions, this stage will perform the `Base + Offset` computation required to determine the memory address to access.

### 4. MEM Stage

The MEM stage is responsible for:

- Reading from or writing a result to memory

All you need to do is to use the value calculated in the EX stage as the address for the RAM. **Note that you must use the maximum address length for the RAM block - this is 16 bits.** To accomplish this, simply take the lower 16 bits of the calculated address. Depending on the instruction, this stage will need to pass either the value read from memory or the value computed in EX to the WB stage.

### 5. WB Stage

The WB stage is responsible for:

- Writing results back to the DPRF (dual-ported register file)

Depending on the instruction, you may need to write a value back to a register. To do this, your WB stage will attach to the data in and write enable inputs of the DPRF in ID/RR. Remember that the DPRF can write **and** read different registers **in the same clock cycle**, which is why WB and ID/RR can share the same register file. For instructions that do not write a register, your WB stage may not do anything at all.

## 4 General Advice

### Subcircuits

For this project, we highly encourage using modular design and creating subcircuits when necessary. We **strongly** recommend using subcircuits when building your pipeline buffers, stages, and forwarding unit. A modular design will make it easier to debug and test your circuit during development.

### Pipeline Buffers

For deciding what to pass through buffers, remember that we need to support the requirements of every possible instruction. Think of what each instruction needs to fulfill its duty, and pass a union of all those requirements. (By union we mean the mathematical union, for example say I1 needs PC and Rx, while I2 needs Rx and Ry, then you should pass PC, Rx and Ry through the buffer). You can also feel free to implement your hardware such that you re-use space in the buffer for different purposes depending on the instruction, but this is not required.

### Control Signals

In the Project 1 datapath, recall that we had one main ROM that was the single source of all the control signals on the datapath. Now that we are spreading out our work across different stages of the pipeline, you have a choice of how to implement your signals!

The first thing to note is that in a pipelined processor, each stage is like a simple one-cycle processor that can do exactly ONE thing intended for that stage in a single cycle. In this sense, there is really no need for a control ROM anymore! Therefore in real processors, each stage of the pipeline is implemented using hardwired control as discussed in Chapter 3 of the textbook. However, to keep your design simple for debugging and getting it working, we are going to suggest using a control ROM to generate the needed control signals for the different independent stages of the pipelined processor.

There are two options:

1. You can either have a single large main ROM in ID/RR which calculates all the control signals for every stage.

**OR**

2. you can have a small(er) ROM or decoders in each stage which takes in the opcode/bits of the opcode and assert the proper signals for that operation.

Note that if you choose the first method, you will need to collect and pass all the control signals needed for later stages through the buffers of earlier stages, and in the second method, you will need to pass the instruction opcode through all the stages so that you can decode it in each stage to assert the signals needed for that stage.

### Stalling

One must stall the pipeline when an instruction cannot proceed to the next stage because a value is not yet available to an instruction. This usually happens because of a data hazard. For example, consider two instructions in the following program:

1. LW \$t0, 5(\$t1)
2. ADDI \$t0, \$t0, 1

Without stalling the ADDI instruction in the ID/RR stage, it will get an out of date value for \$t0 from the regfile, as the correct value for \$t0 isn't known the LW reaches the MEM stage! Therefore, we must stall. Consult the textbook (or your notes) for more information on data hazards.

To stall the pipeline, the stages preceding the stalled stage should disable writes into their buffers, i.e. they should continue to output the previous value into the next stage. The stalled stage itself will output NOOP (example, ADD \$zero, \$zero, \$zero) instructions down the pipeline until the cause of the stall finishes.

## Data Forwarding

Note that you may eliminate a good deal of stalls by implementing data forwarding. This allows the ID/RR stage to retrieve values computed in later stages of the pipeline early so that stalling the instruction is not necessary. It is strongly recommended that you not use the busy bit/read pending bit strategy suggested in the book - this has some very nasty edge cases and requires much more logic than necessary.

It is recommended that you use the provided forwarding unit or make your own that implements various stock rules. The forwarding unit should take in the two register values you read from the DPRF, the output value from the EX stage, the output value from the MEM stage, and the output value from the WB stage.

To forward a value from a future stage back to ID/RR, you must check to see if the destination register number from a particular stage is equal to your source register numbers in the ID/RR stage. If so, you must forward the value from that stage to your ID/RR stage. If multiple stages can forward a value, the stage closest to ID/RR takes priority (EX > MEM > WB).

Note, forwarding cannot save you from one situation: when the destination register of a LW instruction is the source register of an instruction immediately after it. In this case, sometimes called "load-to-use", you must stall the instruction in the ID/RR stage. It is your job to flesh out all of the stall and forwarding rules.

**Keep in mind:** the zero register can never change, therefore it should not be considered for forwarding and stalling situations. The forwarding unit provided already accounts for this, so don't worry about it unless you plan on implementing your own.

## Branch Prediction

Since all of the branching instructions are resolved in EX, the pipeline may be unsure of which instructions are correct to fetch. We could stall fetching further instructions until resolution, but this is inefficient and naive. To better handle control hazards, we can "predict" which instruction could be correct.

For this project we will be predicting the **branch is not taken**, and so the pipeline will continue fetching sequentially. Upon resolving the branch, the pipeline should continue normally in the case of a correct prediction, or flush the incorrectly fetched instructions in the case of an incorrect prediction.

## Flushing the Pipeline

For the BEQ/BLT/JALR instructions, we calculate the target in the EX stage of the pipeline. However, the next two instructions the IF stage fetches while EX is computing the target may not be the next instructions we want to execute. When this happens, we must have a hardware mechanism to "cancel" or "flush" the incorrectly-fetched instructions after we realize they are incorrect.

In implementing your flushing mechanism, it is **highly recommended** that you avoid the asynchronous clear feature of registers in CircuitSim, as this may cause timing issues. Instead, we suggest using a multiplexer to selectively send a NOOP into the buffer input.

## 5 Testing

When you have constructed your pipeline, you should test it instruction by instruction to see if you have all the necessary components to ensure proper execution.

Be careful to only use the instructions listed in the appendix - there are some subtle points in having a separate instruction and data memory. Load the assembled program into both the instruction memory and the data memory and let your processor execute it. Any writes to memory will only affect the data memory.

We have also included a test program that you may assemble and run on your pipeline.

- **pow.s** is the standard power function that you used in P1 to test your processor. You can change the BASE and EXP label values and it should always calculate  $(\text{BASE})^{\text{EXP}}$

The simulator has also been included in the `assembly/` directory. This is the same one from Project 1 which will allow you to run your own assembly programs after they have been assembled. For instructions on this, please see `assembly/README.md`

## 6 Grading

You may receive **up to 3 points of extra credit on your final grade** by completing this project.

- **1 Point:** All stages of the pipeline have been implemented with all required components and connections visible.
- **1 Point:** Your pipeline produces the correct output when running our test program.
- **1 Point:** Your pipeline correctly implements register forwarding. Note, you may design a pipeline without register forwarding, but it will not receive this point.

Due to the late deadline, we cannot accept regrade requests for this project.

## 7 Deliverables

Please submit your completed circuitsim file (**LC-901p.sim**) to Gradescope.

**Always re-download your assignment from Gradescope after submitting to ensure that all necessary files were properly uploaded. If what we download does not work, you will get a 0 regardless of what is on your machine.**

## 8 Appendix A: LC-901 Instruction Set Architecture

The LC-901 is a simple, yet capable computer architecture. The LC-901 combines attributes of both ARM and the LC-2200 ISA defined in the Ramachandran & Leahy textbook for CS 2200.

The LC-901 is a **word-addressable, 32-bit** computer. **All addresses refer to words**, i.e. the first word (four bytes) in memory occupies address 0x0, the second word, 0x1, etc.

All memory addresses are truncated to 16 bits on access, discarding the 16 most significant bits if the address was stored in a 32-bit register. This provides roughly 64 KB of addressable memory.

### 8.1 Registers

The LC-901 has 16 general-purpose registers. While there are no hardware-enforced restraints on the uses of these registers, your code is expected to follow the conventions outlined below.

Table 1: Registers and their Uses

Register Number	Name	Use	Callee Save?
0	\$zero	Always Zero	NA
1	\$at	Assembler/Target Address	NA
2	\$v0	Return Value	No
3	\$a0	Argument 1	No
4	\$a1	Argument 2	No
5	\$a2	Argument 3	No
6	\$t0	Temporary Variable	No
7	\$t1	Temporary Variable	No
8	\$t2	Temporary Variable	No
9	\$s0	Saved Register	Yes
10	\$s1	Saved Register	Yes
11	\$s2	Saved Register	Yes
12	\$k0	Reserved for OS and Traps	NA
13	\$sp	Stack Pointer	No
14	\$fp	Frame Pointer	Yes
15	\$ra	Return Address	No

1. **Register 0** is always read as zero. Any values written to it are discarded. **Note:** for the purposes of this project, you must implement the zero register. Regardless of what is written to this register, it should always output zero.
2. **Register 1** is used to hold the target address of a jump. It may also be used by pseudo-instructions generated by the assembler.
3. **Register 2** is where you should store any returned value from a subroutine call.
4. **Registers 3 - 5** are used to store function/subroutine arguments. **Note:** registers 2 through 8 should be placed on the stack if the caller wants to retain those values. These registers are fair game for the callee (subroutine) to trash.
5. **Registers 6 - 8** are designated for temporary variables. The caller must save these registers if they want these values to be retained.
6. **Registers 9 - 11** are saved registers. The caller may assume that these registers are never tampered with by the subroutine. If the subroutine needs these registers, then it should place them on the stack and restore them before they jump back to the caller.

7. **Register 12** is reserved for handling interrupts. While it should be implemented, it otherwise will not have any special use on this assignment.
8. **Register 13** is your anchor on the stack. It keeps track of the top of the activation record for a subroutine.
9. **Register 14** is used to point to the first address on the activation record for the currently executing process.
10. **Register 15** is used to store the address a subroutine should return to when it is finished executing.

## 8.2 Instruction Overview

The LC-901 supports a variety of instruction forms, only a few of which we will use for this project. The instructions we will implement in this project are summarized below.

Table 2: LC-901 Instruction Set

	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
ADD	0000									DR																							SR2
NAND	0001									DR																							SR2
ADDI	0010									DR																							immval20
LW	0011									DR																							offset20
SW	0100									SR																							offset20
BEQ	0101									SR1																							offset20
JALR	0110									RA																							unused
HALT	0111																																unused
BLT	1000									SR1																							offset20
LEA	1001									DR																							PCoffset20
INC	1111									DR																							unused

### 8.2.1 Conditional Branching

Conditional branching in the LC-901 ISA is provided via two instructions: the BLT ("branch if less than") and BEQ ("branch if equal") instructions. The BEQ will branch to address "incrementedPC + offset20" only if SR1 and SR2 are equal. However, BLT will branch to address "incrementedPC + offset20" only if SR1 is strictly less than SR2.

## 8.3 Detailed Instruction Reference

### 8.3.1 ADD

#### Assembler Syntax

ADD DR, SR1, SR2

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0000	DR	SR1	unused																												SR2

#### Operation

DR = SR1 + SR2;

#### Description

The ADD instruction obtains the first source operand from the SR1 register. The second source operand is obtained from the SR2 register. The second operand is added to the first source operand, and the result is stored in DR.

### 8.3.2 NAND

#### Assembler Syntax

NAND DR, SR1, SR2

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0001	DR	SR1	unused																												SR2

#### Operation

DR = ~(SR1 & SR2);

#### Description

The NAND instruction performs a logical NAND (AND NOT) on the source operands obtained from SR1 and SR2. The result is stored in DR.

**HINT:** A logical NOT can be achieved by performing a NAND with both source operands the same.

For instance,

NAND DR, SR1, SR1

...achieves the following logical operation:  $DR \leftarrow \overline{SR1}$ .



### 8.3.3 ADDI

#### Assembler Syntax

ADDI DR, SR1, immval20

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0010				DR				SR1				immval20																			

#### Operation

DR = SR1 + SEXT(immval20);

#### Description

The ADDI instruction obtains the first source operand from the SR1 register. The second source operand is obtained by sign-extending the immval20 field to 32 bits. The resulting operand is added to the first source operand, and the result is stored in DR.

### 8.3.4 LW

#### Assembler Syntax

LW DR, offset20(BaseR)

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0011				DR				BaseR				offset20																			

#### Operation

DR = MEM[BaseR + SEXT(offset20)];

#### Description

An address is computed by sign-extending bits [19:0] to 32 bits and then adding this result to the contents of the register specified by bits [23:20]. The 32-bit word at this address is loaded into DR.

### 8.3.5 SW

#### Assembler Syntax

SW SR, offset20(BaseR)

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0100				SR				BaseR				offset20																			

#### Operation

MEM[BaseR + SEXT(offset20)] = SR;

#### Description

An address is computed by sign-extending bits [19:0] to 32 bits and then adding this result to the contents of the register specified by bits [23:20]. The 32-bit word obtained from register SR is then stored at this address.

### 8.3.6 BEQ

#### Assembler Syntax

BEQ SR1, SR2, offset20

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0101				SR1				SR2				offset20																			

#### Operation

```
if (SR1 == SR2) {
    PC = incrementedPC + offset20
}
```

#### Description

A branch is taken if SR1 and SR2 are equal. If this is the case, the PC will be set to the sum of the incremented PC (since we have already undergone fetch) and the sign-extended offset[19:0].

### 8.3.7 JALR

#### Assembler Syntax

JALR RA, AT

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0	1	1	0	RA																	AT							unused			

#### Operation

RA = PC;

PC = AT;

#### Description

First, the incremented PC (address of the instruction + 1) is stored into register RA. Next, the PC is loaded with the value of register AT, and the computer resumes execution at the new PC.

### 8.3.8 HALT

#### Assembler Syntax

HALT

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0111				unused																											

#### Description

The machine is brought to a halt and executes no further instructions.

### 8.3.9 BLT

#### Assembler Syntax

BLT SR1, SR2, offset20

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1000				SR1				SR2				offset20																			

#### Operation

```
if (SR1 < SR2) {
    PC = incrementedPC + offset20
}
```

#### Description

A branch is taken if SR1 is (strictly) less than SR2. If this is the case, the PC will be set to the sum of the incremented PC (since we have already undergone fetch) and the sign-extended offset[19:0].

### 8.3.10 LEA

#### Assembler Syntax

LEA DR, label

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1001				DR				unused				PCoffset20																			

#### Operation

DR = PC + SEXT(PCoffset20);

#### Description

An address is computed by sign-extending bits [19:0] to 32 bits and adding this result to the incremented PC (address of instruction + 1). It then stores the computed address into register DR.

### 8.3.11 INC

#### Assembler Syntax

INC DR

#### Encoding

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
1111				DR				unused																							

#### Operation

DR = DR + 1;

#### Description

Increments the value stored in register DR by one and stores the computed result into the same register DR.